

# Homework 1

Zach Neveu

January 15, 2020

## 1. Problem 1

```
def divide_by_three(integerlist):  
    """  
    This function outputs a list where, if the integer on  
    the input list is divisible by three, the corresponding  
    output is 1 else the output is 0  
    """  
    return [integerlist[i]%3 == 0 for i in range(len(integerlist))]
```

## 2. Problem 2: full adder

Table 1: Truth table of full adder				
Input 0	Input 1	$C_{in}$	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

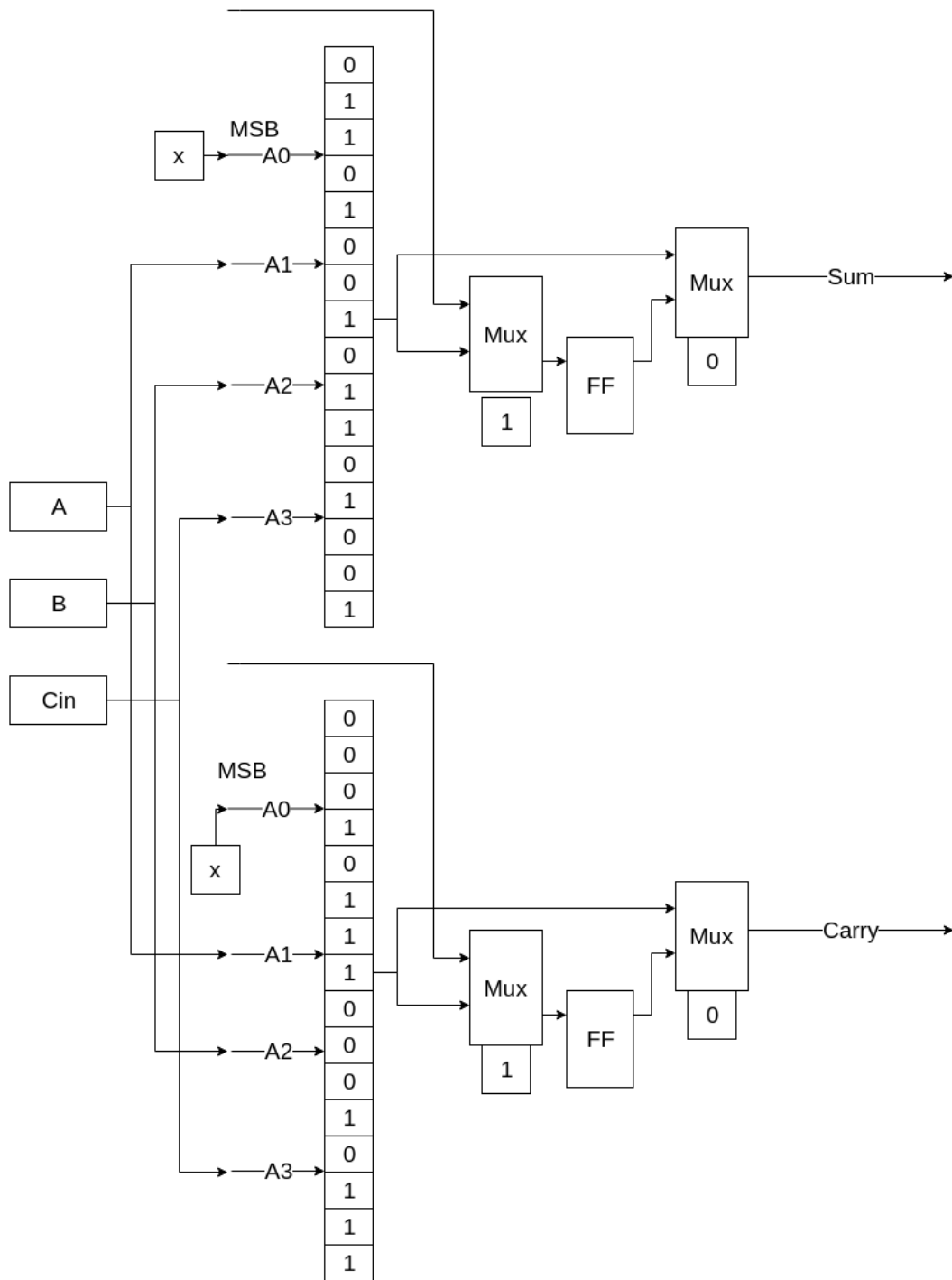


Figure 1: Full Adder on Simplified Logic Slices

### 3. Problem 3: "101" Detector

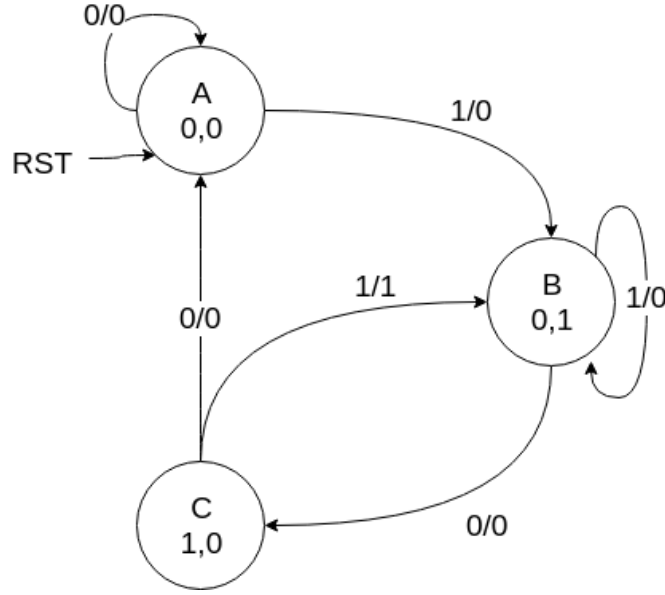


Figure 2: State machine for "101" detector

Table 2: States to binary for "101" recognizer

State	Binary Representation
A	"00"
B	"01"
C	"10"

Table 3: Truth Table for State and Output of "101" detector

Q	A	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>0</sub> <sup>*</sup>	Q <sub>1</sub> <sup>*</sup>	Output
A	0	0	0	0	0	0
B	0	0	1	1	0	0
C	0	1	0	0	0	0
n/a	0	1	1	x	x	x
A	1	0	0	0	1	0
B	1	0	1	0	1	0
C	1	1	0	0	1	1
n/a	1	1	1	x	x	x

$$\begin{aligned}
 Q_0^* &= \bar{x} \wedge \overline{Q_0} \\
 Q_1^* &= x \\
 Output &= x \wedge Q_0.
 \end{aligned} \tag{1}$$

Figure 3: Equations for State and Output of "101" detector

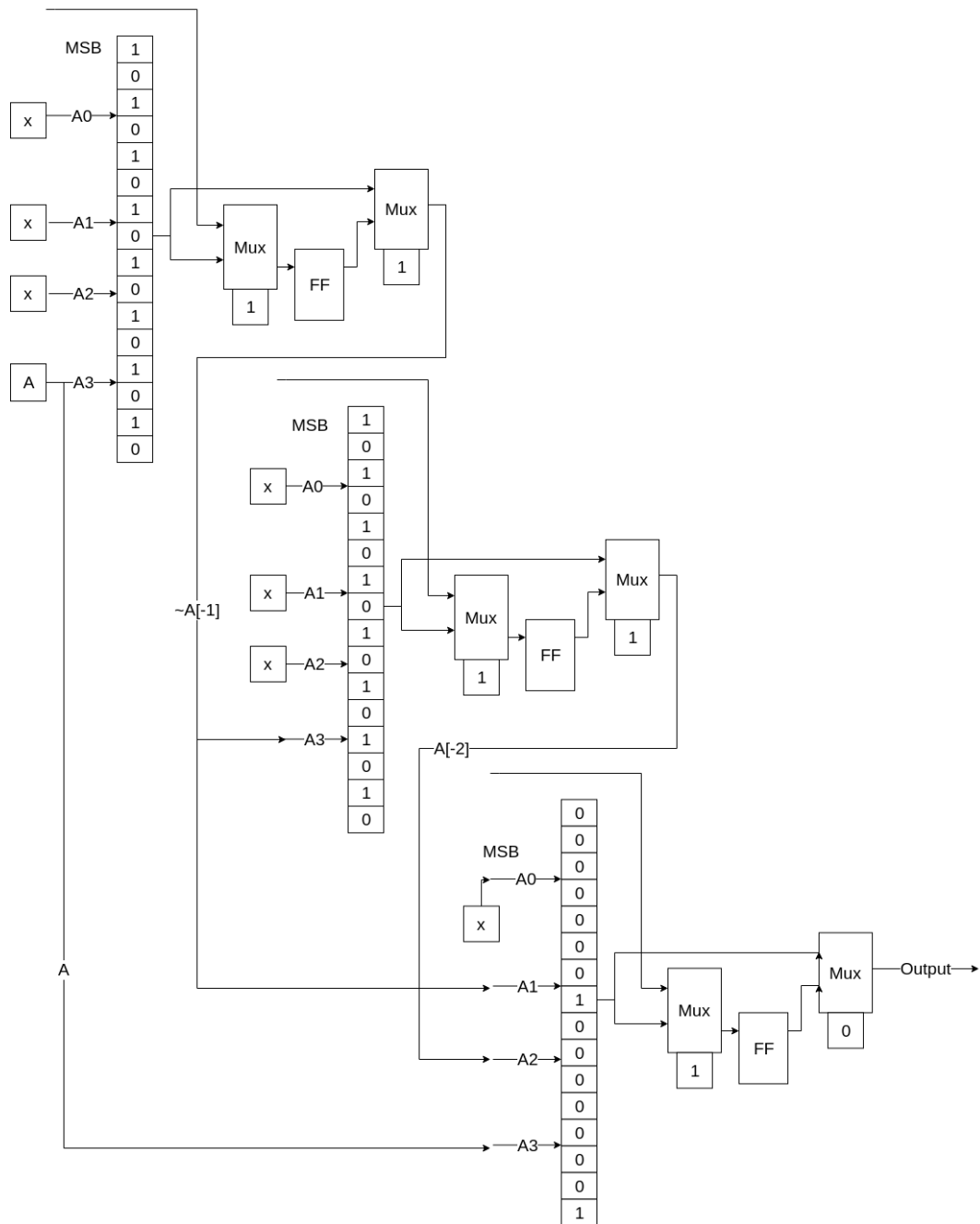


Figure 4: "101" recognizer implemented on simplified logic slices